

Miniproject 1

Marc Eftimie

September 11, 2023

1 Schematics

1.1 Inverter

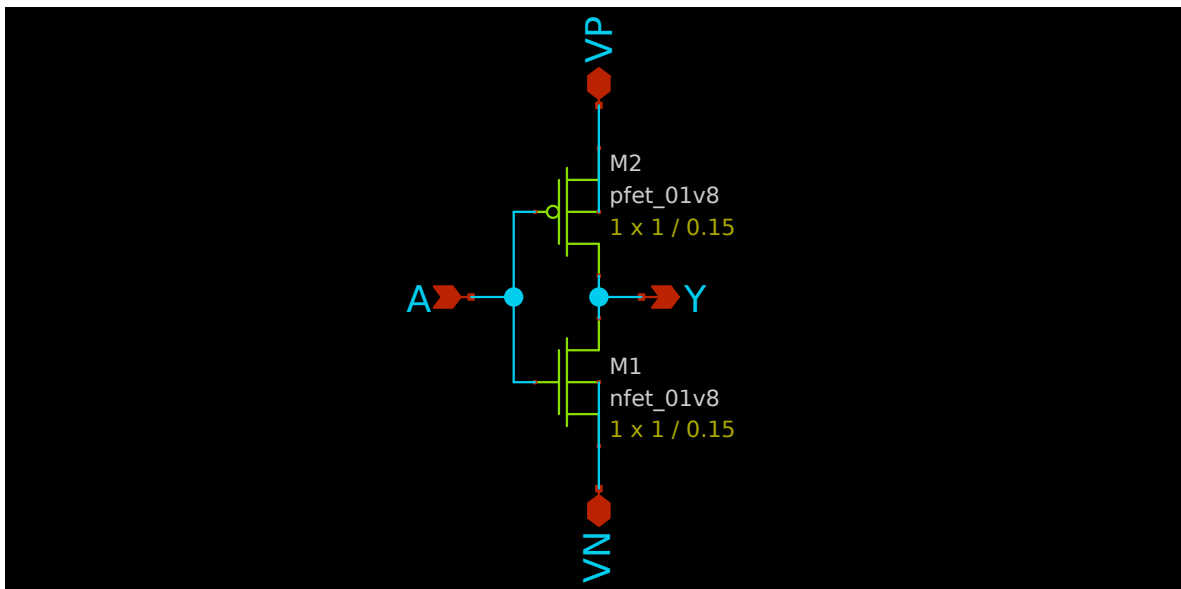


Figure 1: Inverts the signal connected to port A.

1.2 NAND

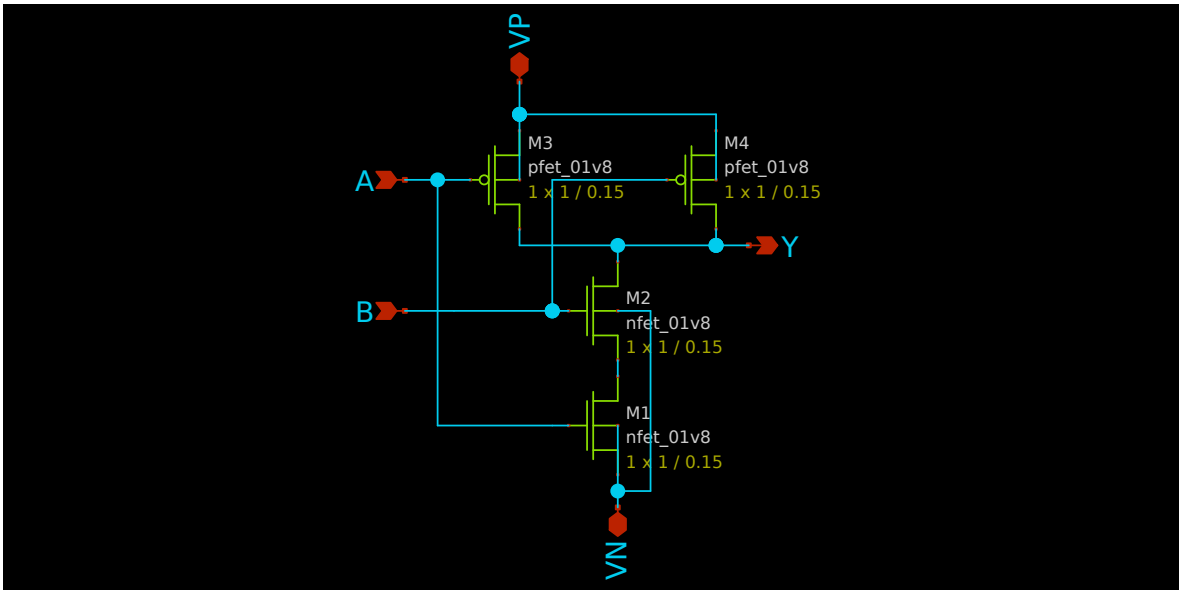


Figure 2: Computed the NAND operation on the signals connected to ports A and B.

1.3 AND

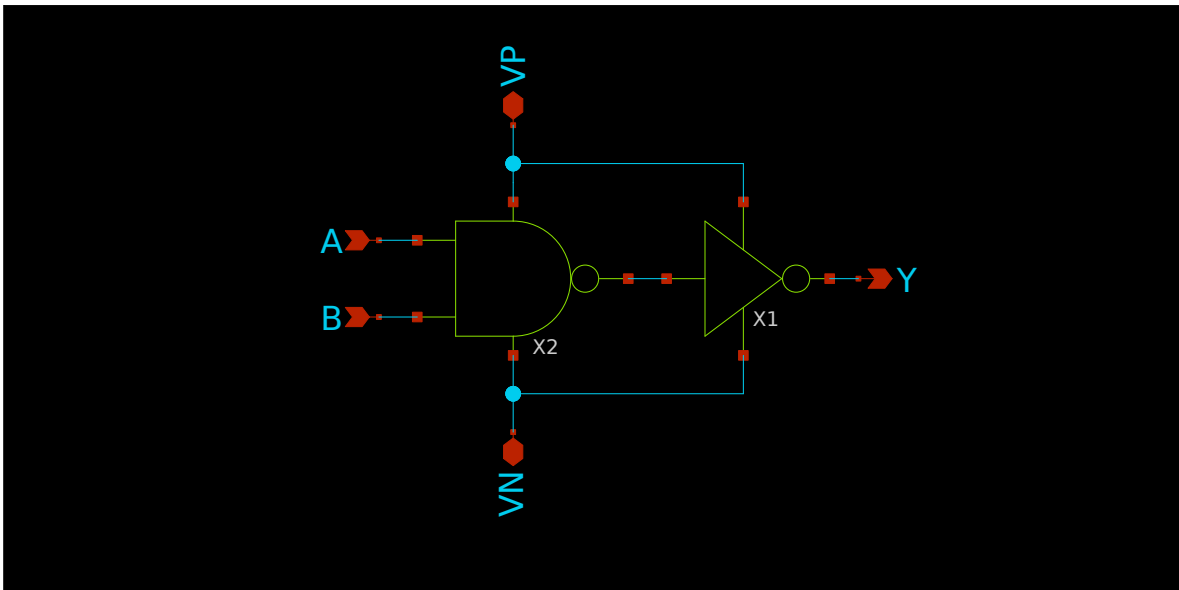


Figure 3: AND logic is obtained by inverting the output of a NAND gate.

1.4 AND Test Harness

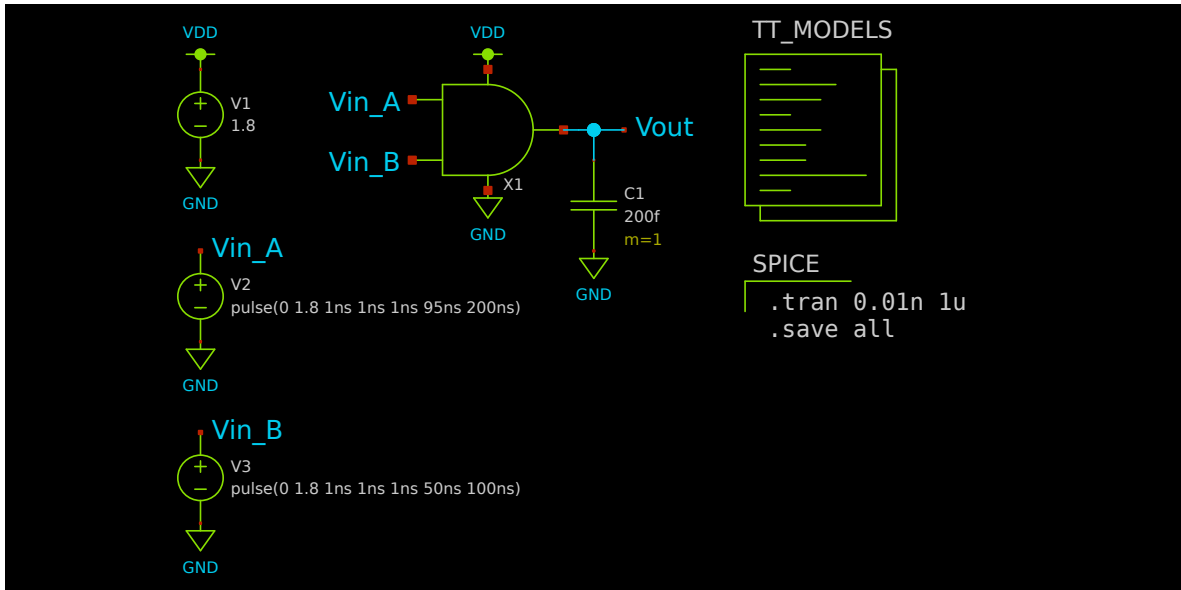


Figure 4: Test harness of the AND gate. Voltage pulses are setup to test all possible inputs for A and B.

2 Transient Plots

2.1 AND Transient

 


Figure 5: The top pain shows the inputs of the AND gate A (blue) and B (red). All permutations of the inputs are tested (00, 01, 10, 11). The bottom pain shows the output of the AND gate Y (blue). The output is high when A and B are high and low at all other times.

3 Layouts

3.1 AND Layout

 


Figure 6: NAND gate (left) is abutted to an inverter (right) to create a AND gate.

4 Layout Vs Schematic

4.1 LVS Comparison Output

Listing 1: Command output

```
1
2 Circuit 1 cell sky130_fd_pr__pfet_01v8 and Circuit 2 cell
   sky130_fd_pr__pfet_01v8 are black boxes.
3 Equate elements: no current cell.
4 Device classes sky130_fd_pr__pfet_01v8 and sky130_fd_pr__pfet_01v8 are
   equivalent.
5
6 Circuit 1 cell sky130_fd_pr__nfet_01v8 and Circuit 2 cell
   sky130_fd_pr__nfet_01v8 are black boxes.
7 Equate elements: no current cell.
8 Device classes sky130_fd_pr__nfet_01v8 and sky130_fd_pr__nfet_01v8 are
   equivalent.
9
10 Subcircuit summary:
11 Circuit 1: inverter                                |Circuit 2: inverter
```

12	----- -----	
13	sky130_fd_pr__pfet_01v8 (1)	sky130_fd_pr__pfet_01v8 (1)
14	sky130_fd_pr__nfet_01v8 (1)	sky130_fd_pr__nfet_01v8 (1)
15	Number of devices: 2	Number of devices: 2
16	Number of nets: 4	Number of nets: 4
17	----- -----	
18	Netlists match uniquely.	
19		
20	Subcircuit pins:	
21	Circuit 1: inverter	Circuit 2: inverter
22	----- -----	
23	Y	Y
24	A	A
25	VP	VP
26	VN	VN
27	----- -----	
28	Cell pin lists are equivalent.	
29	Device classes inverter and inverter are equivalent.	
30		
31	Subcircuit summary:	
32	Circuit 1: nand	Circuit 2: nand
33	----- -----	
34	sky130_fd_pr__pfet_01v8 (2)	sky130_fd_pr__pfet_01v8 (2)
35	sky130_fd_pr__nfet_01v8 (2)	sky130_fd_pr__nfet_01v8 (2)
36	Number of devices: 4	Number of devices: 4
37	Number of nets: 6	Number of nets: 6
38	----- -----	
39	Netlists match uniquely.	
40		
41	Subcircuit pins:	
42	Circuit 1: nand	Circuit 2: nand
43	----- -----	
44	VP	VP
45	B	B
46	A	A
47	VN	VN
48	Y	Y
49	----- -----	
50	Cell pin lists are equivalent.	
51	Device classes nand and nand are equivalent.	
52		
53	Subcircuit summary:	
54	Circuit 1: and.spice	Circuit 2: and_xschem.spice
55	----- -----	
56	inverter (1)	inverter (1)
57	nand (1)	nand (1)
58	Number of devices: 2	Number of devices: 2
59	Number of nets: 6	Number of nets: 6
60	----- -----	
61	Netlists match uniquely.	
62	Cells have no pins; pin matching not needed.	
63	Device classes and.spice and and_xschem.spice are equivalent.	

```
64 |
65 | Final result: Circuits match uniquely.
66 |
```